

GATE QUESTION Q36

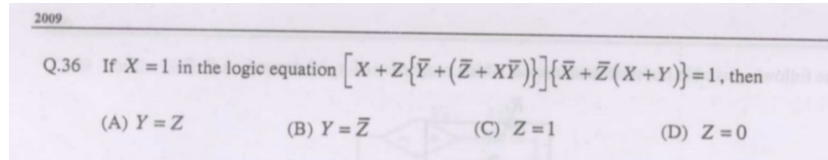


Figure 1: GATE Question Q36

Contents

1	Components	2
2	Boolean Simplification	2
3	Hardware Connections	2
4	Software Implementation	2
5	Output	3
6	Result	3

1 Components

Breadboard

Arduino Uno

IC 7447

Seven Segment Display

Jumper Wires

2 Boolean Simplification

The simplified K-Map expression is

$$A = \bar{W}\bar{Z}$$

The remaining outputs are

$$B = 0, \quad C = 0, \quad D = 0$$

When $W = 0$ and $Z = 0$,

$$A = 1$$

Hence the display shows 1.

3 Hardware Connections

Arduino Pin D6 is connected to W.

Arduino Pin D7 is connected to X.

Arduino Pin D8 is connected to Y.

Arduino Pin D9 is connected to Z.

Arduino Pin D2 is connected to A of IC 7447.

Arduino Pin D3 is connected to B of IC 7447.

Arduino Pin D4 is connected to C of IC 7447.

Arduino Pin D5 is connected to D of IC 7447.

Arduino Pin D13 is used as Clock.

4 Software Implementation

```
#include <Arduino.h>
int W,X,Y,Z;
int D,C,B,A;
```

```

void disp_kmap(int D,int C,int B,int A)
{
    digitalWrite(2,A);
    digitalWrite(3,B);
    digitalWrite(4,C);
    digitalWrite(5,D);
}

void setup()
{
    pinMode(2,OUTPUT);
    pinMode(3,OUTPUT);
    pinMode(4,OUTPUT);
    pinMode(5,OUTPUT);
    pinMode(6,INPUT);
    pinMode(7,INPUT);
    pinMode(8,INPUT);
    pinMode(9,INPUT);
    pinMode(13,OUTPUT);
}

void loop()
{
    digitalWrite(13,HIGH);
    delay(10);
    digitalWrite(13,LOW);

    W = digitalRead(6);
    X = digitalRead(7);
    Y = digitalRead(8);
    Z = digitalRead(9);

    A = !W & !Z;
    B=0; C=0; D=0;

    disp_kmap(D,C,B,A);
    delay(1000);
}

```

5 Output

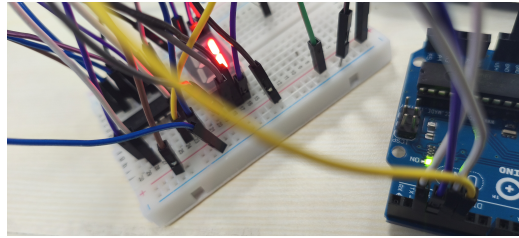


Figure 2: Output Showing 1

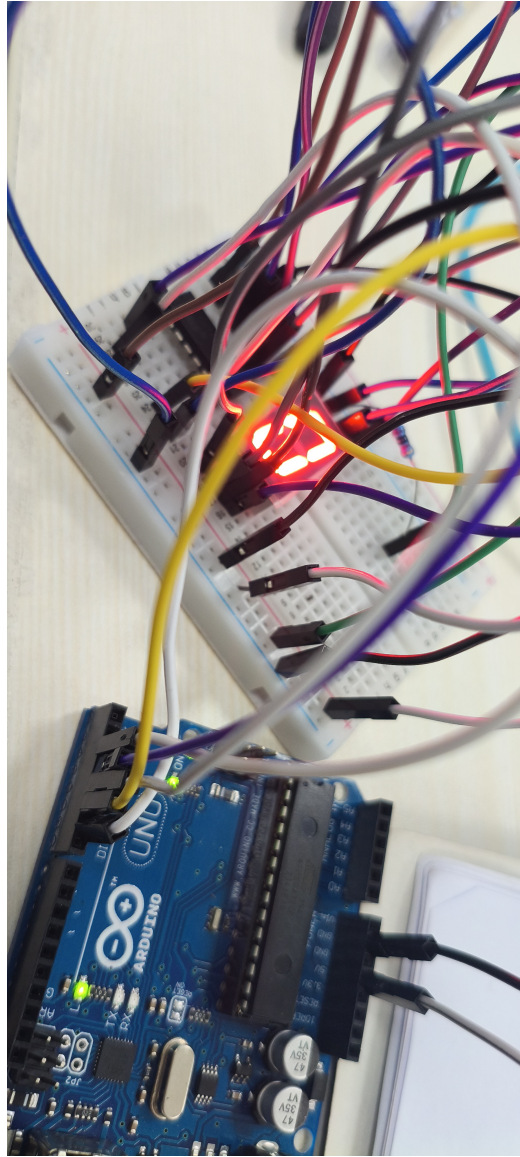


Figure 3: Output Showing 0

The Karnaugh Map expression was implemented using Arduino Uno and IC 7447.

$$A = \bar{W}\bar{Z}$$

For $W = 0$ and $Z = 0$,

$$A = 1$$

Therefore the seven segment display shows 1.